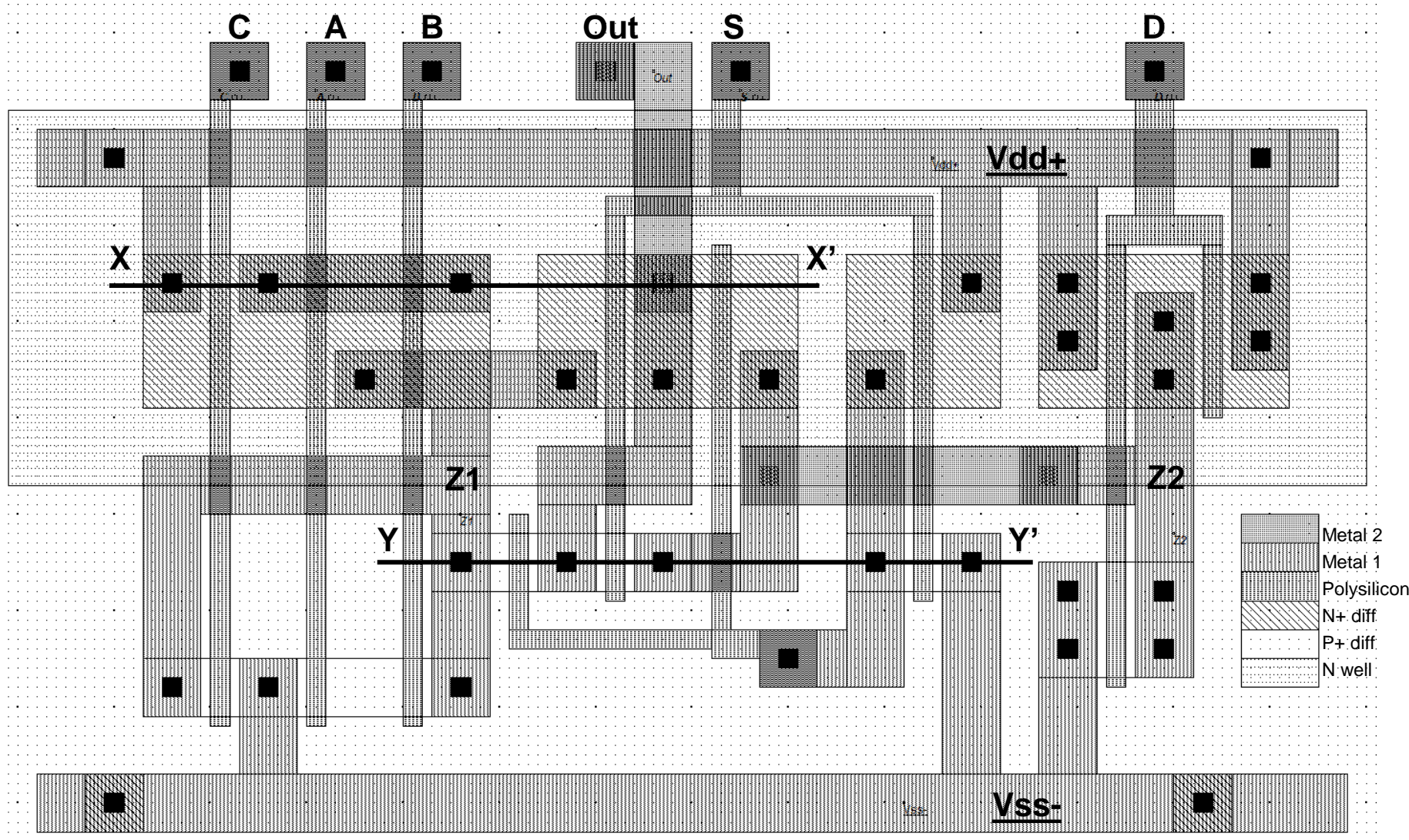


Problem 1 (50 min, 4 pt)

The figure shows the layout of a digital circuito, where A, B, C, D and S are inputs, Out is output and Z1 and Z2 are intermediate signals.


- a) List the layers forming the contacts on the Vdd and Vss lines and explain the purpose of these contacts
- b) Draw the transistor schematic from the layout
- c) Draw the logic function of the intermediate signals Z1 and Z2, and the Out output
- d) Draw the circuit gate schematic
- e) Draw the cross section of XX' and YY' cuts



Problema 2 (30 min, 3 pto)

A digital circuit has a clock input driving 1560 flip-flops (FFs). We assume each FF shows a parasitic capacitance equivalent to that of a minimum size inverter.

 a) Calculate the delay and area of a single-stage tree, such as the one in the figure as a function of the delay (t_{pi}) and area (A_0) of the minimum size inverter (W).




b) Calculate the delay and the area of a clock tree where the maximum *fanout* is 2.

c) The inverter in the figure is to be replaced by a chain of inverters of increasing size. Indicate the number of inverters required for a minimum delay, the delay obtained, and the required area.

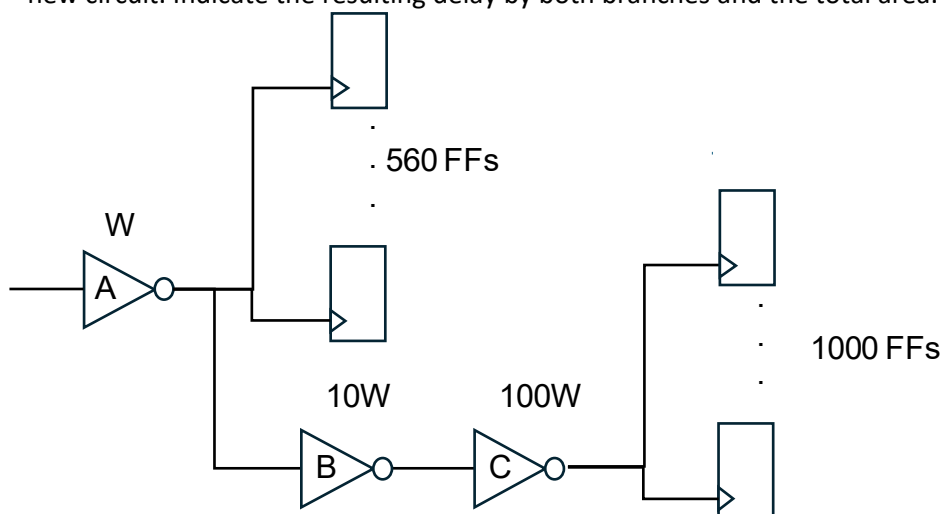
d) The circuit is modified as shown in the figure.

- Indicate how long it takes for inverter A to switch
- Indicate the delay from inverter A output to inverter C output
- Propose a solution to include a pair of inverters of size βW and ϕW in the 560 FFs branch, in order to reduce the delay of inverter A and to balance the delay by the two branches of the new circuit. Indicate the resulting delay by both branches and the total area.



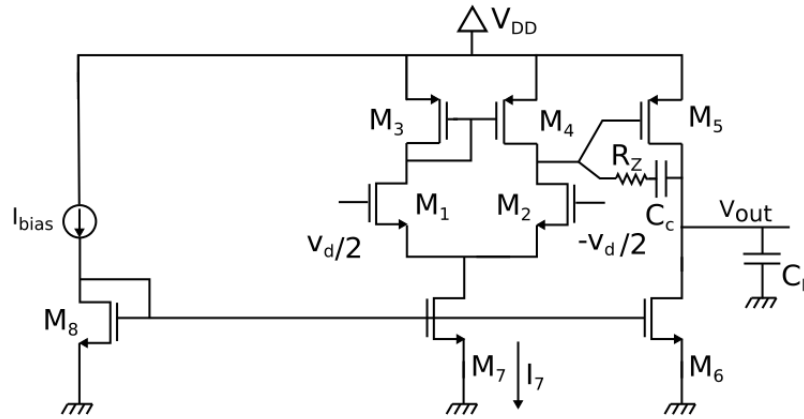Problema 3 (30 min, 2.5 pto)

An operational amplifier like the one depicted in the figure will be designed, with differential input and single-ended output.



The requirements to accomplish are listed below:

- **Power consumption of 120 μW** (the three branches are included. It is assumed that the three branches consume the same). $V_{DD} = 1\text{ V}$.
- a) Set the current I_{bias} considering the transistors M_6 , M_7 and M_8 similar (0.5 pts).
- **Minimum and maximum output voltages of 0.2 V and 0.8 V**, respectively.
- b) Use the previous requirement to define (W/L) of M_5 and M_6 (0.5 pts).
- **Gain-Bandwidth product higher or equal than 100 MHz.**
- c) Use the previous requirement to define (W/L) of M_1 and M_2 (0.5 pts).
- d) Compute the gain of the operational amplifier (V_{out}/V_d) (0.5 pts).
- e) Justify the operating point of transistor M_8 (0.5 pts).

Data and equations:

$$\mu_P C_{ox} = 45 \mu\text{A}/\text{V}^2 \quad \lambda_P = 0.3 \text{ V}^{-1} \quad V_{thp} = -0.3 \text{ V}$$

$$\mu_N C_{ox} = 90 \mu\text{A}/\text{V}^2 \quad \lambda_N = 0.6 \text{ V}^{-1} \quad V_{thn} = 0.3 \text{ V}$$

$$C_L = 1 \text{ pF}, C_c = 0.5 \text{ pF}, L = 200 \text{ nm (for all the transistors)}$$

$$GBW = \frac{g_{m1}}{2\pi C_C}$$